

Printed By: Technical And Vocational College

Date: 24.07.2025 11:00 AM

061004T4ICT

#### **ICT TECHNICIAN LEVEL 5**

IT/OS/ICT/CC/01/5 ted By: Technical And Vocational College

Apply Basic Elect  ${}^{\mathrm{D}}\mathbf{r}^{\mathrm{a}}\mathbf{o}^{\mathrm{te}}\mathbf{n}^{\mathrm{-}}\mathbf{i}^{\mathrm{2}}\mathbf{c}^{\mathrm{4}}\mathbf{s}^{\mathrm{07.2025}}$  11:00 AM

July/August 2025

Printed By: Technical And Vocational College Day, 4 07 2025

11:00 AM

TVET CURRICULUM DEVELOPMENT, ASSESSMENT AND CERTIFICATION COUNCIL

Printed By: Technical And Vocational College Date: 24.07.2025

# TVET CURRICULUM DEVELOPMENT, ASSESSMENT AND CERTIFICATION COUNCIL (TVET CDACC)

11:00 AM

## WRITTEN ASSESSMENT

Printed By: Technical And Vocational College

Date: 24.07.2025 11:00 AM Time: 3 HOURS

## INSTRUCTIONS TO CANDIDATE

Printed By: Technical And Vocational College

Date: 24.07.2025 11:00 AM

- 1. The paper consists of **TWO** sections: **A** and **B**.
- 2. Answer all questions in section A and ANY THREE (3) questions in section B.
- 3. Marks stion are in dicated in the backets
- 4. Candidates are provided with a separate answerirbookyleetu Technical And Vocational College
- 5. **DO NOT** write on the question paper.

Date: 24.07.2025 11:00 AM

Printed By: Technical And Vocational College Date: 24.07.2025 11:00 AM

Printed By And Vocational College

Candidate should check the question paper to ascertain that all pages are printed as indicated and that no questions are missing.




Printed By: Technical And Vocational College

Date: 24.07.2025 11:00 AM

#### **SECTION A (40 MARKS)**

## Answer ALL the questions in this section.

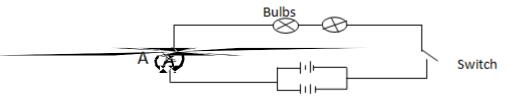- 1. A technician in irae com it he illustrating it he difference between NPN and PNP Bipolar Data size to 25 to 00 a An administrator. Using simple diagrams illustrate the structure of NPN and PNP Bipolar Transistor. (4 marks)
- 2. Give the difference between semiconductor from optical memory technologies by Printed By: Technical And Vocational College outlining, their main properties and functions (2 marks)
- 3. The figure below shows a circuit diagram with cells in parallel. Each cell has e.m.f. of Printed By: Technical And Vocational College 1.5V and internal resistance of  $0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the  $r_Destination is taken to the substitution of <math>0.5\Omega$  and the substitution is taken to the substitution of  $0.5\Omega$  and the substitution is taken to the substitution of  $0.5\Omega$  and the substitution is taken to the substitution of  $0.5\Omega$  and the substitution is taken to the substitution of  $0.5\Omega$  and the substitution is taken to the substitution of  $0.5\Omega$  and the substitution is taken to the substitution of  $0.5\Omega$  and the substitution



- 4. Computers have various interrelated components that work together to ensure they Printed By: Technical And Vocational College Date: 2d4e.0l7iv.2e0r2s5 i1t1s: 0 m/and ate. Name the function of each of the following electronic components found in computers.
  - a) Signal diodes
  - b) Capacitors

Printed By: Technical And ( $\sqrt{2}$ 0 c  $\hat{m}$ 1  $\hat{a}$ 0  $\hat{r}$ 1  $\hat{k}$ 2  $\hat{s}$ 3 ollege Date: 24.07.2025 11:00 AM

- 5. Temperature of a material plays a key role in the electrical conductivity; give the effects of temperature in extrinsic semiconductors. (2 marks)
- 6. Perform the following number conversions:

Printed By: Technical And Vocational College

- a) 135 (hexadecimal) to Binary Printed By: And V (o2 a moa a k Cso) lege
- b) 126 (decimal) to Hexadecimal Date: 24.07.2025 11:00 AM

(2 marks)

(2 marks)


- c) 1001001(Binary) to Decimal (2
- d) 1434 (Octal) to Bin Technical And Vocational College Date: 24.07.2025 (2 marks)
- 7. Draw a diagram to show how you would use a Zener diode in a circuit. (2 marks)
- 8. Junction diodes are widely used in electronic circuits due to their ability to control the Princedeinge near thicklower. V Bransced coornegy our understanding, list TWO common uses of Date:

  2julin no 7c · t2i 0o2n5 1d1 ii 0o0d Ae M. (2 marks)
- 9. The diagram below shows two identical lamps  $L_1$  and  $L_2$  connected to a battery. Outline the effect if any, of closing switch S on  $L_1$  (2 marks)




Printed By: Technical And Vocational College Date: 24.07.2025

11:00 AM

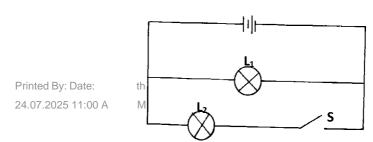

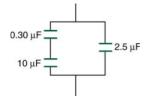- 10. With respect to atomic theory of matter, identify the difference between valence band Printed By: Technical And Vocational College and acconduction bandom (2 marks)
- 11. A computer has programmable memories that are read only and are permanent as Printed By Technical And Vocational College compared to RAM which is temporary. List THREE E7. t2yppesi\_100f0 rAeMad only memory (ROM)

  (3 marks)
- 12. A trainee at technical institution learning about capacitors and circuits. Given the network below, determine; (4 marks)



Printed By: Technical And Date: 24.07.2025 11:00 AM

- i. Total capacitance in parallel C  $_t$  =C1+C2
- ii. Total charge across the circuit if it is connected to a 24V battery.
- 13. Highlight two limitations why digital circuits are inpercent greather can it not estignanal Colege


Date: 24.07.2025 11:00 AM

(2 marks)

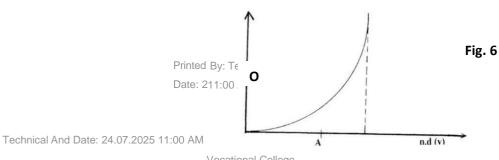14. The Byrape below shows a Torward bias characteristic of a pn junction.

Date: 24.07.2025 11:00 AM

Describe what happens to the depletion layer pasint education and violation and violat



SECTION B (60 MARKS)

# Answer Any THREE Questions in This Section

15. Modern computing systems rely on a combination of electronic components, secure data management, and binary representation to ensure reliable and secure digital operations.

Printed By: Diodes play an important role in electronic circuits, each designed for specific functions. Examine the TWO distinct types of diodes by addressing the following

for each Printed By: And Vocational College

(10 marks)

- Name and a escribe the type of diode. i.
- ii. Explain its mode of formation.
- Analyze its primary function in an electronic circuit. iii.

Printed Technical And Vocational College  $i_2v_4$ .  $i_2v_3$   $i_2v_4$ .  $i_2v_3$   $i_2v_4$ .  $i_2v_3$   $i_2v_4$   $i_$ real-world application.

- b) A newly employed IT technician in an IT company is assigned the role of a data Printed By: Technical And Vocational College administrator within the organization.  $Ex_{1}p_{1}a_{1}in_{2}T_{1}H$   $R_{1}E_{2}E_{1}w_{1}a_{2}y_{3}s_{1}in$  which he will acquire, manipulate and store data against hackers, crackers and data loss. (6 marks)
- c) Computers universally operate using binary rather than other number systems. As an ICT trainee, explain TWO fundamental reasons why binary representation is ideal for data processing and storage in digital systems. (4 marks)
- 16. You are provided with a basic electrical circuit shown in the figure below. The circuit is intended to investigate the relationship between current (I) and voltage (V) in accordance Printed By Technical And Vocational College Date 244 it h 2026

mi's Law. ional College Date: Printed By: And Vocational College ate: 24.07.2025 11:00 AM rheostat a) Describe Ohm's law (2 Marks)

b) Explain two ways in mehich the saddoverify Ohm's law.

(4 Marks)

c) Sketch a graph of  $V^{a}a^{b}e^{a}$   $a^{24}$ in  $^{0}s^{7}t^{2}I^{025}$  11:00 AM

(4 Marks)

d) Using two's complement, work out 3510 – 1710, giving your answer in decimal

notation (5 marks)

Printed By Technical And Vocational College

 $D_{\text{ole}}(e_2)_{407}U_2s_1i_2n_5g_{11}o_1n_2e'_4s_1$  complement subtracts 17 from 28 decimal notations.

(5 mark)

17.

a) With the aid of a diagram explain TWO methods of biasing bipolar junction transistors (BJTS) that he taught them. (6 marks)

©2025TVET\_CDACC



Printed By: And Vocational College Date: 24.07.2025 11:00 AM

- b) Explain TWO challenges an individual could experience when migrating from analogue to digital. (4 marks)
- c) A consumer relection ics coitness educed sales due to changing consumer prefer field of \$25 find 000 ethavior. In particular the consumers prefer more portable devices, smart and cost effective. Advice the management on steps to take to recapture market share.

  Printed By: And Vocational College
- 18. With the 24 on 12 erge new point mobile and computing technologies, modern electronic systems like Smartphones are now being designed with integrated computing capabilities.

  Printed By: Technical And Vocational College
  - a) Explain the statement; a Smartphone is basically an electronic system with similar component to a computer, by assessing FIVE similarities between the Smartphone and computer in relation their feature. (10 Marks)
  - A motherboard is an example of an electronic circuit in computers. In designing an
    electronic circuit, explain THREE components are likely to be put into consideration.
     (6 Marks)
- c) The threat of cyber-attacks continues to be a growing concern for the electronics

  Printed By Technical And Vocational College

  Date: 24.0 in 2000 u fi a cotou/rim g industry. Justify how by explaining TWO major concerns. (4 Marks)

Printed By: And Vocational College Date: 24.07.2025 11:00 AM

Printed By And Vocational College Date: 24.07.2025 11:00 AM

Printed By: And Vocational College Date: 24.07.2025 11:00 AM

Printed By And Vocational College Date: 24.07.2025 11:00 AM

Printed By: Technical And Vocational College Date: 24.07.2025

11:00 AM